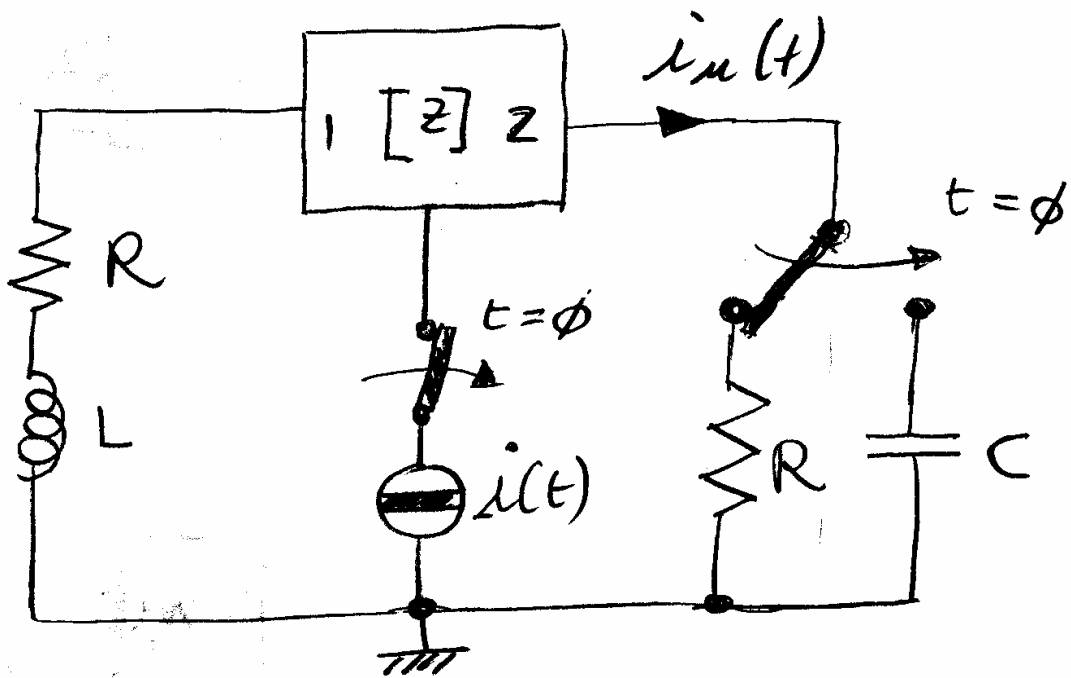




1. Determinare la corrente  $i_u(t)$  per tutto l'asse dei tempi.  $i(t) = \sin(2t)$

$(R=1/2, C=1, L=1 \text{ [A, } \Omega, \text{ F, H]}; [Z]=\begin{bmatrix} 2 & 1 \\ 1 & 1 \end{bmatrix})$ .



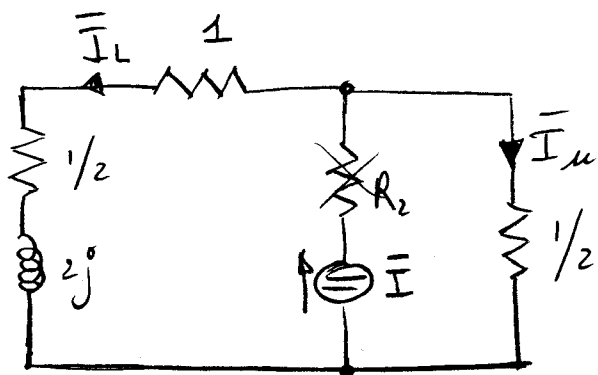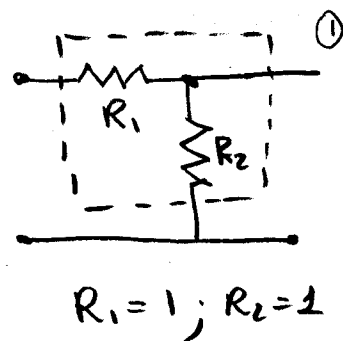
1)  $t < 0$  Foronari

Nota:  $[z] = \begin{bmatrix} 2 & 1 \\ 1 & 1 \end{bmatrix} \Rightarrow$



Nota:  $R_2$  in serie

Calcolo  $\bar{I}_L, \bar{I}_u$

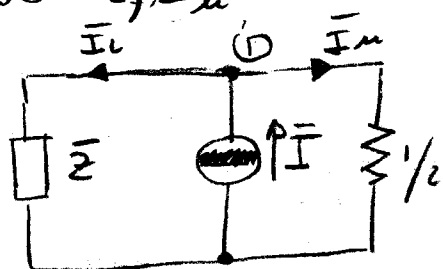

$$\bar{z} = \frac{3}{2} + 2j$$

$$\bar{I} = -j$$

Eq. Nodo ①  $\left[ \frac{1}{\bar{z}} + 2 \right] [\bar{E}_1] = \bar{I} \Rightarrow \bar{E}_1 = \frac{\bar{I}}{2 + 1/\bar{z}} = \frac{\bar{z} \bar{I}}{2\bar{z} + 1}$

$$\bar{I}_u = \frac{\bar{E}_1}{R} = \frac{\bar{z} \bar{I}}{2\bar{z} + 1} = \frac{-2j \left( \frac{3}{2} + 2j \right)}{3 \left( \frac{3}{2} + 2j \right) + 1} = \frac{(4-3j)(4-4j)}{4+4j} = \frac{16-16j-12j-12}{32} = \frac{1}{8} - \frac{7}{8}j$$

$$\Rightarrow \boxed{i_u(t) = \sqrt{\frac{25}{32}} e^{00(2t - \arctan(7))} \quad t < 0}$$


KCL ①  $\rightarrow$

$$\bar{I}_L = \bar{I} - \bar{I}_u = -j - \frac{1}{8} + \frac{7}{8}j = -\frac{1}{8} - \frac{1}{8}j = \frac{1}{\sqrt{32}} e^{j \arctan(1)} \Rightarrow$$

$$i_L(t) = \frac{1}{\sqrt{32}} e^{00(2t + \pi/4)}$$

$$i_L(0) = \frac{1}{\sqrt{32}} e^{00(\pi/4)} = \frac{1}{8}$$

$t \gg \phi$

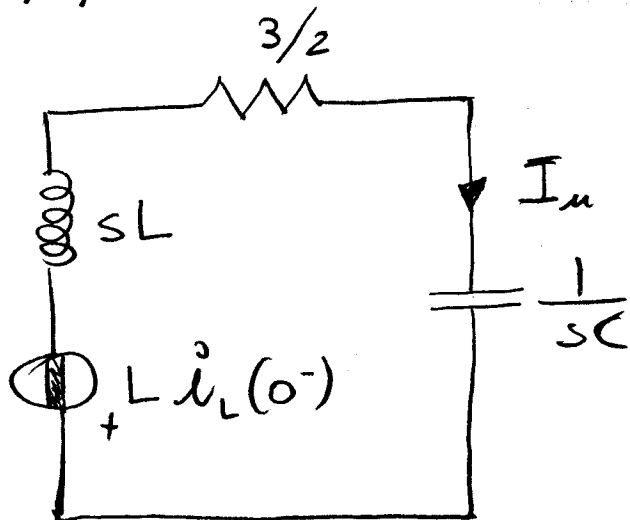

$$I_m(s) = \frac{L i(0^-)}{R + sL + \frac{1}{sC}} = \frac{-1/8}{\frac{3}{2} + s + \frac{1}{s}} = \frac{s/8}{s^2 + \frac{3}{2}s + 1}$$
$$= \frac{r e^{j\theta}}{s + \alpha - j\omega} + \frac{r e^{-j\theta}}{s + \alpha + j\omega} \Rightarrow$$

$$\begin{aligned} r &= 0.094 \\ \theta &\cong \pi/4 \\ \alpha &= \frac{3}{4} \\ \omega &= \sqrt{\frac{7}{16}} \end{aligned}$$

$$i_m(t) = r e^{j\theta} e^{-(\alpha - j\omega)t} + r e^{-j\theta} e^{-(\alpha + j\omega)t} \Rightarrow$$

$$i_m(t) = 2r e^{-\alpha t} \cos(\omega t + \theta) \Rightarrow$$

$$i_m(t) = -0.189 e^{-\frac{3}{4}t} \cos\left(\sqrt{\frac{7}{16}}t + \frac{\pi}{4}\right)$$