
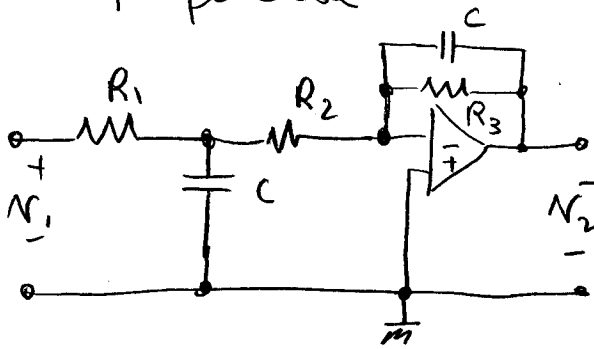


calcolare la  $F(s) = \frac{V_2(s)}{V_1(s)}$  del circuito in figura e  
tracciare l'andamento qualitativo delle risposte  
in frequenza


$R_1=1, R_2=2, R_3=3, C=1$  [Ω,F]

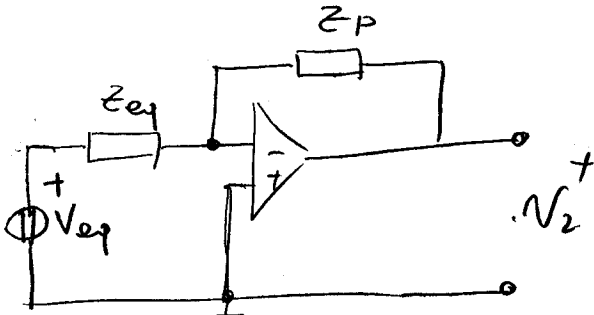

Il circuito è un ampli. invertente del tipo:


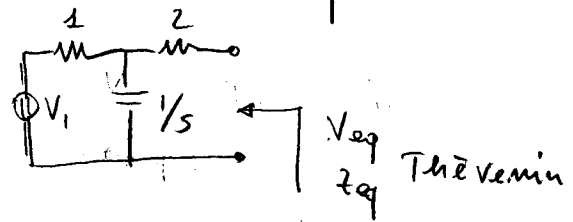
$$V_2 = - \frac{Z_p}{Z_{eq}} \cdot V_{eq}$$




$$Z_p = \frac{1}{sC} \parallel R_3 = \frac{3}{s+3}$$

$$Z_{eq} = \left( R_1 \parallel \frac{1}{sC} \right) + R_2 = \frac{1}{1+s} + 2 = \frac{3+2s}{1+s}$$

$$V_{eq} = \frac{V_1}{R_1 + \frac{1}{sC}} \cdot \frac{1}{sC} = \frac{V_1}{s+1}$$
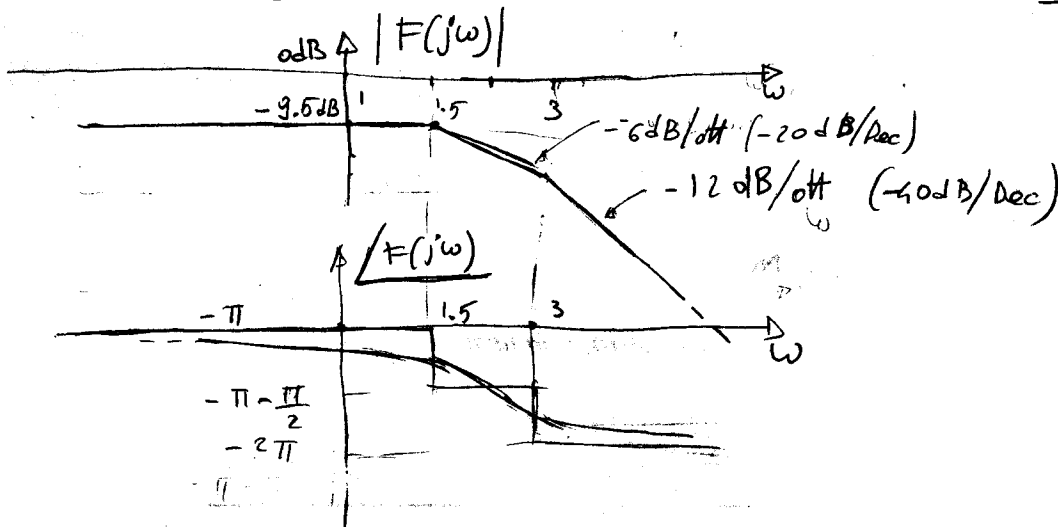
$$F(s) = \frac{V_2}{V_1} = - \frac{3}{(s+3)(2s+3)} = - \frac{1}{3} \frac{1}{\left(1 + \frac{1}{3}s\right)\left(1 + \frac{2}{3}s\right)}$$



$$\tau_1 = \frac{1}{3}$$

$$\tau_2 = \frac{2}{3}$$