


\bar{Z}_x tale da avere
max transf. pot.

$$V_g(t) = e \cos(t)$$

$$R_1 = 1, R_2 = \frac{1}{2} [\Omega]$$


$$C = 1 [F] \quad L = 2 [H]$$

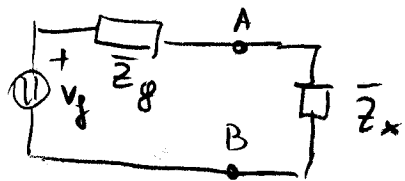la condizione di max transf. pot.
è verificata se



$$\bar{Z}_x = \bar{Z}_g^*$$

• calcolo \bar{Z}_g ($\omega = 1$)

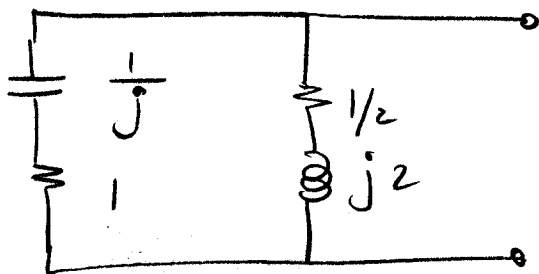

$$\bar{Z}_g = (1 - j) // \left(\frac{1}{2} + j2 \right) = \frac{21 - j}{13}$$

$$\Rightarrow \bar{Z}_x = \frac{21 + j}{13}$$